



## **lab report 5**

Andrew Nady

900184042

## Question 1

### Technical summary

#### Steps:

- In the experiment 1, we added in the source code some testcases, then we wrote the testbench to test the code.
- In experiment 2, we wrote the testbench that can write and then read from the data memory

```
mem[0]=32'd17;  
mem[1]=32'd9;  
mem[2]=32'd25;  
mem[3]=32'd55;  
mem[4]=32'd40;
```

#### Functionalities:

- In experiment 1, it is the instruction memory which will contain the instructions that will be implemented and executed.
- In experiment 1, it is the Data memory which will contain some data that were stored and we can load any data from it

#### Components:

- Verilog
- VNC


## Question 2:

### Code:

- Note: I attached all the code in a separate folder

### Question 3: Results


#### Exp1:

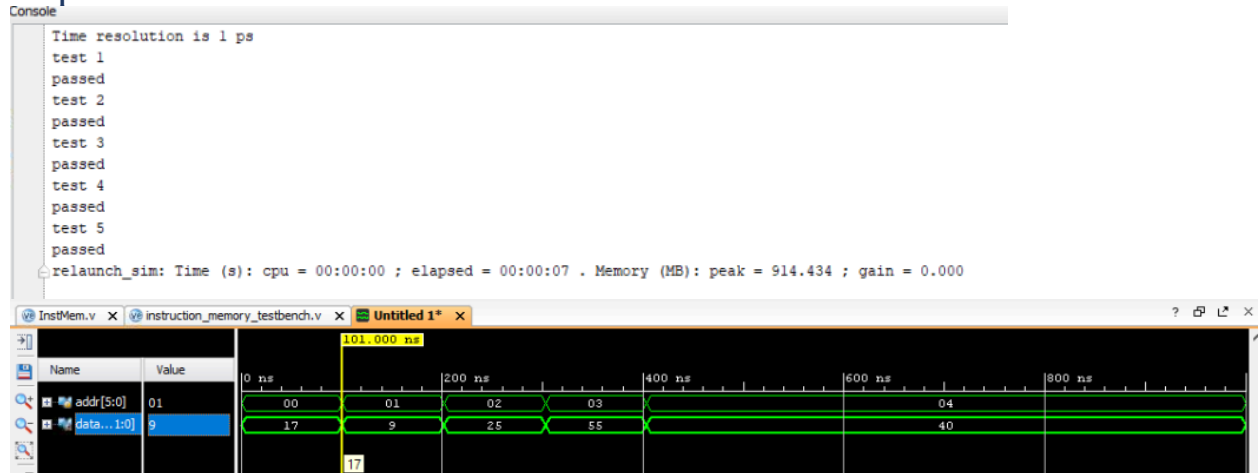

- As I told later that we added 5 test cases in the source file and in the testbench we tried to read them and we successfully read them.

```
mem[0] = 32'd17;
mem[1] = 32'd9;
mem[2] = 32'd25;
mem[3] = 32'd55;
mem[4] = 32'd40;
```

#### Exp2:

 

- We wrote in the data memory using writing flags 5 times with 5 different values
- Then we tried to read them all again, and we successful read and wrote them correctly.

## Question 4: Exercise 3

```
`timescale 1ns / 1ps
module Full_dataPath( input clk, input rst );
wire [31:0] PCin, PCout0, PCout1, PCmux;
wire cout1_ripple1, cout1_ripple2;
wire [31:0] ints_out;
wire [31:0] readdata1, readdata2 ;
reg [31:0] gen_out; //should be reg || wire
reg branch;
reg memread;
reg memtoreg;
reg [1:0] aluop;
reg memwrite;
reg alusrc;
reg regwrite;
reg [3:0] aluS;
wire [31:0] outmux_input_alu;
reg [31:0] ALU_result;
wire zero;
wire [31:0] dataMem_out;
wire [31:0] writingData;
wire [31:0] shiftout;
//instantiate 32bitreg PCin PCout

ripple_carry ripplecar0(PCin,
32'd4,
0,
PCout0,
cout1_ripple1
);
//adder tany
ripple_carry ripplecar1(PCin,
shiftout,
0,
PCout1,
cout1_ripple2
);

//mux
ThirtytwoMUX mux3(PCout0, PCout1, branch & zero, PCmux);
//register (PCmux, PCin) //reload the PC
//instmem
```

```

InstMem instmem(PCin[7:2],ints_out);
//control unit
Control_unit controlunit(ints_out[6:0], branch,
    memread, memtoreg,
    aluop, memwrite, alusrc, regwrite );
//alu_control
ALU_Control aluControl(aluop, ints_out[14:12],ints_out[30],aluS);
//registerfile
RegisterFile regfile( clk, rst,
    ints_out[19:15], ints_out[24:20], ints_out[11:7],
    writingData,
    regwrite,
    readdata1, readdata2 );
//immGenerator
immediate_generator immgen( gen_out, ints_out );
//shifting left
shiftLeft( gen_out , shiftout );
//mux
ThirtytwoMUX mux (readdata2,gen_out,alusrc ,outmux_input_alu);
//ALU
ALU alu(
    readdata1, outmux_input_alu,
    aluS,
    ALU_result, zero );
//dataMem
DataMem datamem( clk, memread, memwrite,
    ALU_result[7:2], readdata2, dataMem_out);
//mux after the datamem
ThirtytwoMUX(dataMem_out,dataMem_out,memtoreg ,writingData);
endmodule

```

- We still need to add a register for the PC
- And modify some parts that we used the PC as not a register